

Tiny Trainable Instruments - User Guide

Materials


Participants of the study will get these 6 minimum materials for building your Tiny Trainable Instruments:

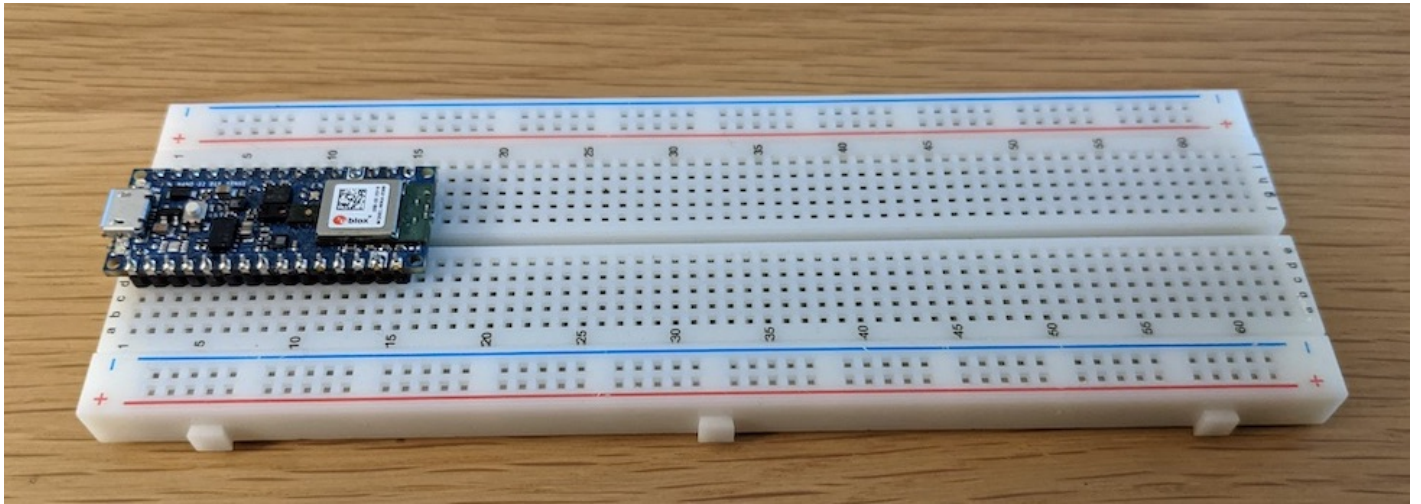1. 1x Arduino Nano 33 BLE Sense microcontroller with headers
2. 1x Micro USB Cable
3. 1x Solderless breadboard
4. 1x Pack of jumper wires
5. 1x Micro servo motor
6. 1x Piezo buzzer




Assembly


During the workshop, we will place the Arduino microcontroller on the solderless breadboard, to make all the connections in a safe and easy way.



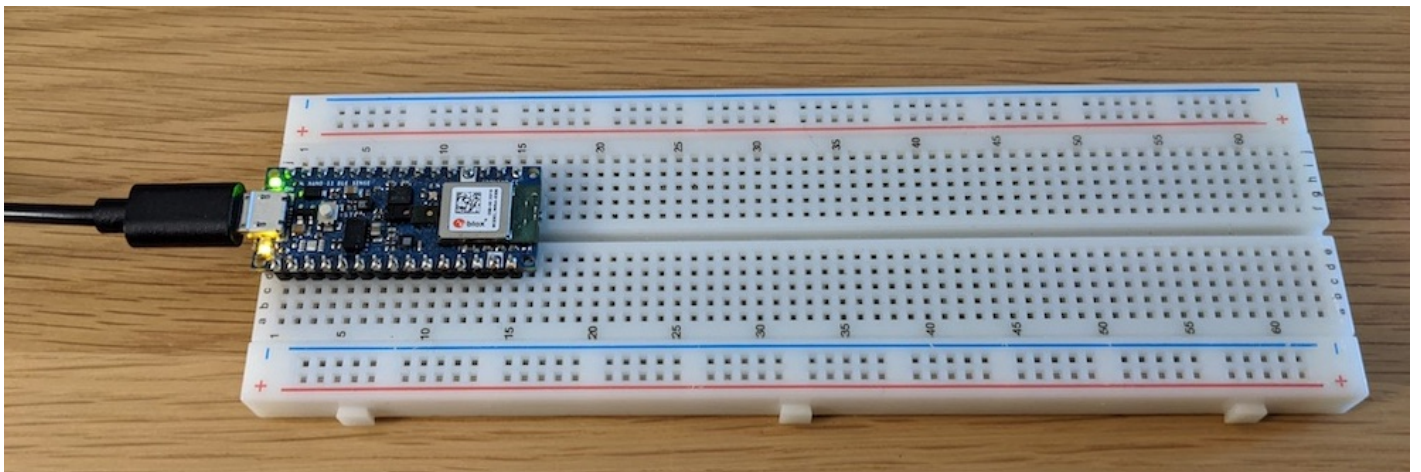We will use the USB cable to both power our circuits and to be able to upload code from our computers. When the Arduino microcontroller is powered on, its LEDs light up.



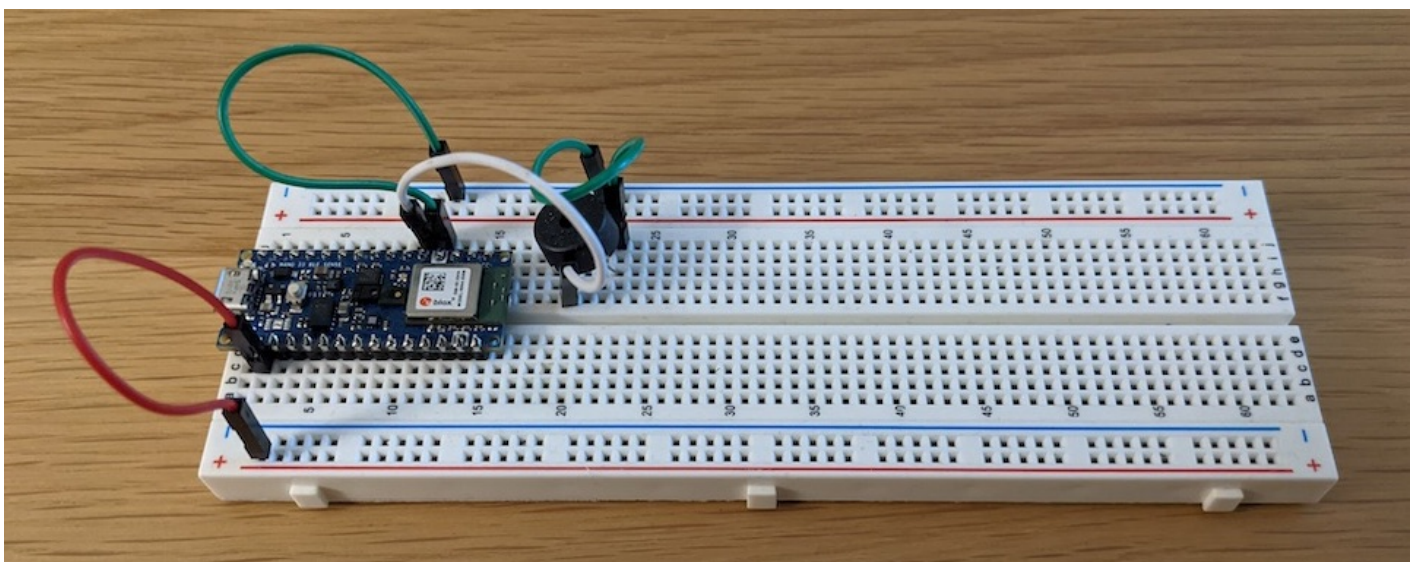During the workshop we will assemble 2 circuits: the first one involves the piezo buzzer, and it involves 4 jumper wires.



The other circuit is for the servo motor and it involves 8 jumper wires.

