Wiring

Conventions

Wires:

- Red = 3.3 V power from Arduino
- Green = Ground from Arduino

Breadboard

Breadboards are built so that within each of the rows, the 5 tie points in the columns labelled a-e are electrically connected inside the board and act as a single electrical node, and same with f-j.

Adicionalmente, hay 2 columnas a cada lado de la protoboard, donde cada columna está interconectada entre sí. Convencionalmente, conectamos el voltaje positivo a la columna +, y tierra a la columna -.


In addition, there are 2 columns to each side of the breadboard, where each column is one electrical node. Conventionally, we connect the positive voltage to the column labelled +, and the ground to the column labelled -.

A full breadboard guide is available at https://learn.adafruit.com/breadboards-for-beginners/breadboards.


Arduino microcontroller

The ArduinoNano BLE 33 Sense we are using has 30 pins in total, 15 on each side. The official pinout is available at https://content.arduino.cc/assets/Pinout-NANOsense_latest.pdf.

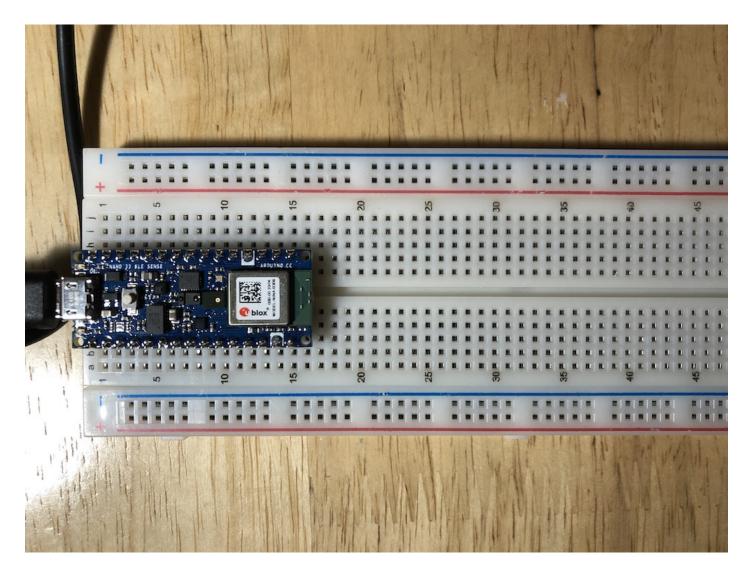We recommend placing the microcontroller at the top of the breadboard (C1 to C15 and G1 to G15) with the USB Micro port facing up.



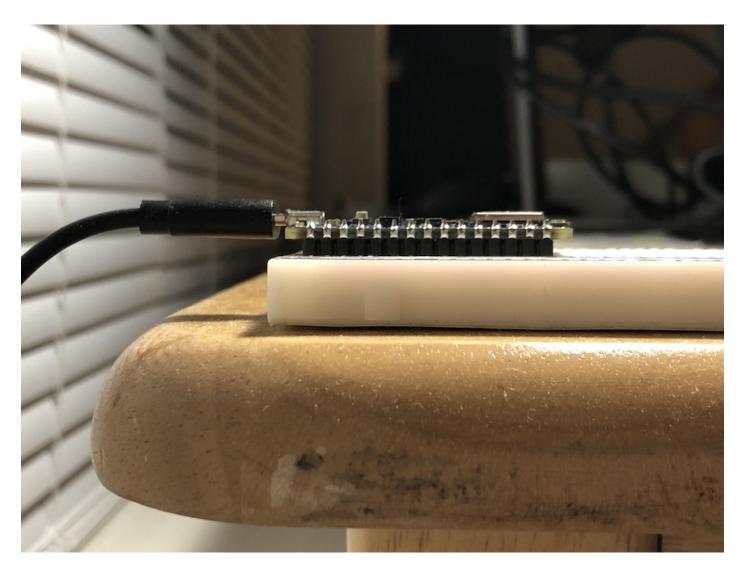Note that the microcontroller should be flush with the breadboard; none of the headers should be visible.



Your first example

Connect your Arduino microcontroller to your computer with the USB cable and open the Arduino IDE software.


On the board, select the Arduino Nano 33 BLE.




Then make sure yor port points to your Arduino, the number is irrelevant, and the actual text changes between computers.



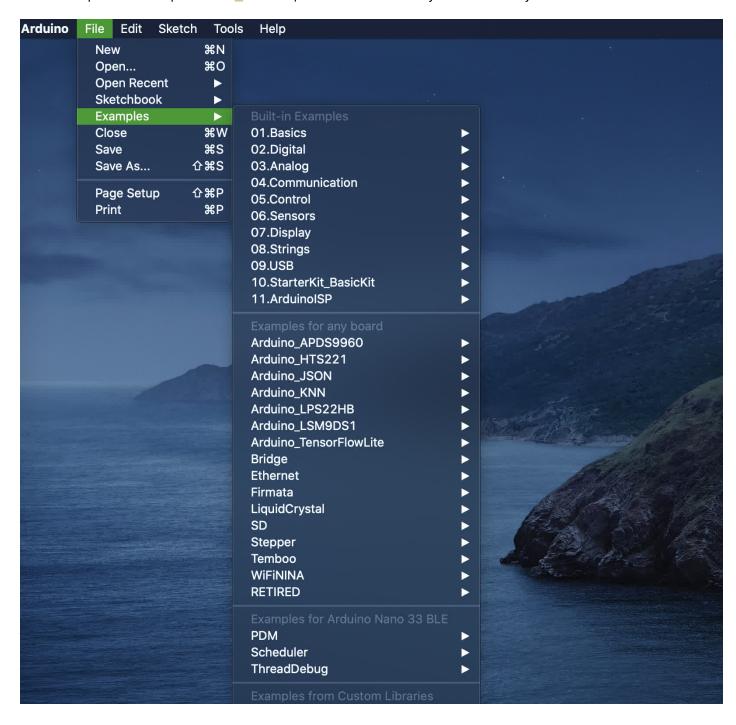Now let's open the example check_serial, included with our TinyTrainable library.



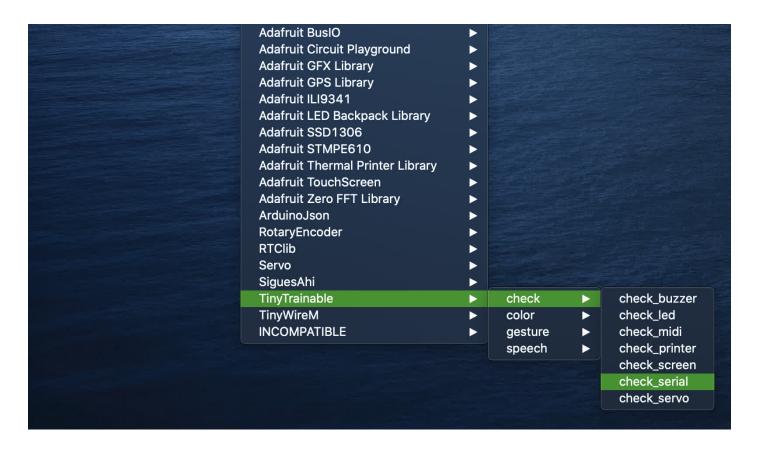

Click on the arrow to the right for uploading the code, which will be shown on the bottom of the Arduino IDE, with the message Compiling sketch.

```
my i iny . set StateLEDBul Ltin(true);
29
30
    delay(pauseTime);
31
    myTiny.setStateLEDBuiltIn(false);
32
    delay(pauseTime);
33
34
    // cycle through the 6 colors of the RGB LED
35
    myTiny.setStateLEDRGB(true, red);
    delay(pauseTime);
36
    my Time cottatal EDDCDCtore anonal.
```

```
Compiling sketch...

ResolveLibrary(SPI.h)
-> candidates: [SPI]
/Users/montoyamoraga/Library/Arduino15/packages/arduino/tools/arm-none-eabi-gcc/7-2017q4/bin/arm-r
Alternatives for Adafruit_GFX.h: [Adafruit_GFX_Library@1.10.10]

ResolveLibrary(Adafruit_GFX.h)
-> candidates: [Adafruit_GFX_Library@1.10.10]
/Users/montoyamoraga/Library/Arduino15/packages/arduino/tools/arm-none-eabi-gcc/7-2017q4/bin/arm-r
Alternatives for Adafruit_SSD1306.h: [Adafruit_SSD1306@2.4.5]


ResolveLibrary(Adafruit_SSD1306.h)
-> candidates: [Adafruit_SSD1306.02 4 5]
```

The compilation might take several minutes, and after it is done, the message will change to Uploading...

This process is shorter, and after it you will see the message Done uploading.

```
35
     myTiny.setStateLEDRGB(true, red);
36
     delay(pauseTime);
     myTime cotCtatal EDDCDCtana
Done uploading.
                                      (108/114 pages)write(addr=0x34,size=0x1000)
 iteBuffer(scr.
 iteBuffer(scr_add
                                                    es)write(addr=0x34,size=0x100
 iteBuffer(scr_add
 riteBuffer(scr
                                                         ite(addr=0x34,size=0x100
 riteBuffer(scr_c
riteBuffer(scr_add
                               =7 100% (114/114 pages)
 ne in 18.200 seconds
 eset()
```

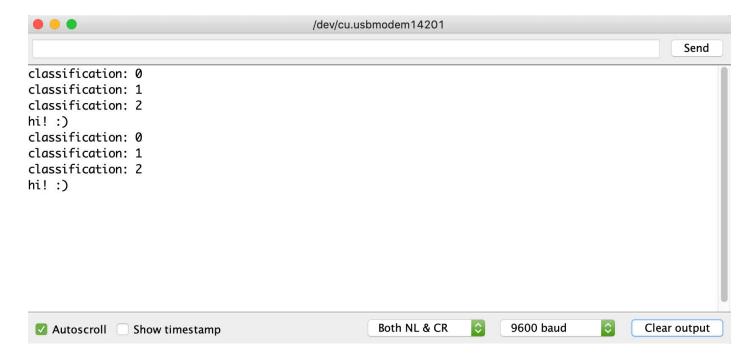On the upper right corner of the window, click on the magnifying glass icon for opening the Serial monitor. Make sure the settings on the bottom match the ones on your computer, and that's it!




You uploaded your first example to your Arduino, which is now busy sending the messages you seen on the screen, and also showing all the different lights it has:)

Outputs

Buzzer

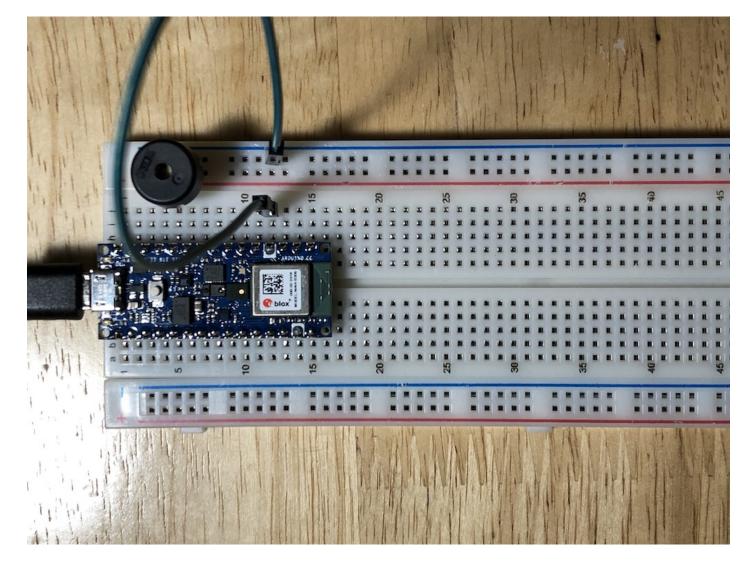For the next example, check_buzzer, we'll need to install a piezo buzzer. First, notice that the 14th pin on the left side and the 12th pin on the right side are labelled with white paint; this marks ground, also identified on the pinout. Take a wire (preferably green by convention for ground) and connect it from I12 to anywhere on the top righthand negative rail (the upper 25 pins), like this:



Next, connect one of the legs of the piezo buzzer to the node labelled D8 on the pinout (which should be row 5 on the breadboard). Connect the other leg to the ground rail. Your wiring should look like this:

Installing the piezo buzzer

Now you're good to go! Upload check_buzzer to the microcontroller, open the serial monitor (top right button in the Arduino IDE), and follow the instructions from there!

LED

MIDI

MIDI Din jack

5 pins, only 3 are used.

Printer

We are using a thermal printer from Adafruit.

https://www.adafruit.com/product/2753

It has 5 cables:

VH - red - connect to the power supply 5V - 9V DTR - yellow - connect to GND on the Arduino TX - green - data out of the printer RX - blue - data in to the printer GND - black - connect to GND on the Arduino

We use a power supply, whose ground is connected to the one on the Arduino.

The power supply is 9V, center positive. Here is one available: https://www.adafruit.com/product/276

Serial

With a serial cable into a computer.